

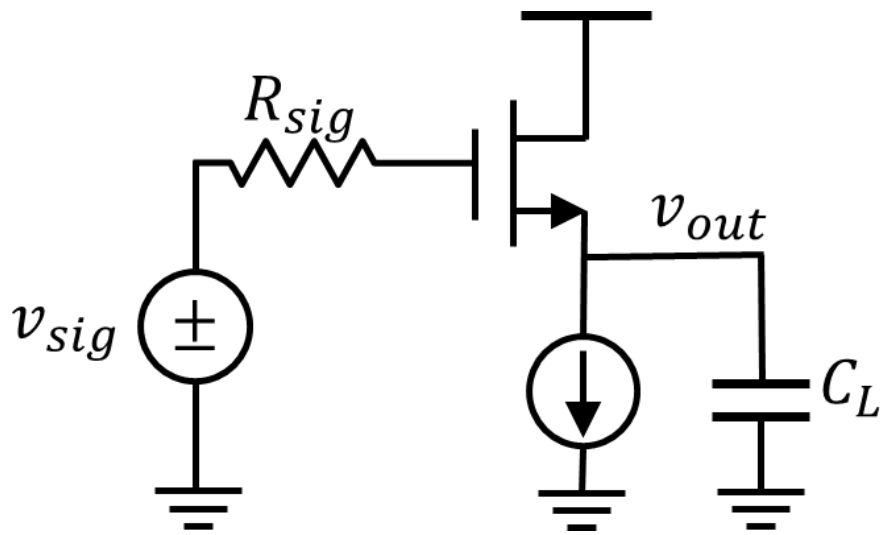


Frequency Response of CD

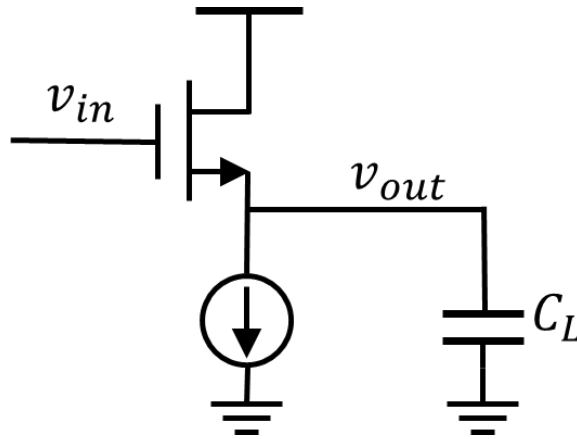

- ❑ The circuit has two poles.
- ❑ C_{gs} is bootstrapped.
- ❑ The two poles are nearby and possibly complex conjugate.
- ❑ we can't use the OCTC technique and Miller approximation directly.


divide and conquer

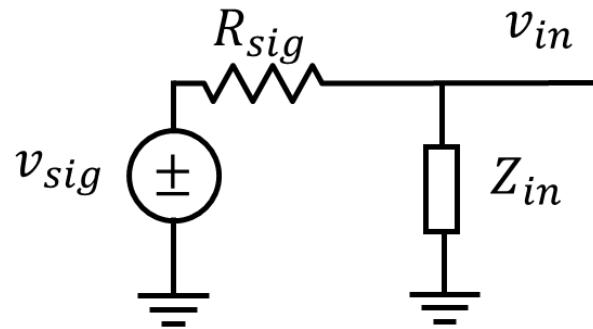

$$\square \frac{v_{out}}{v_{sig}} = \frac{Z_{in}}{Z_{in} + R_{sig}} \frac{v_{out}}{v_{in}}$$

□ now all we need is to find v_{out}/v_{in} and Z_{in}

v_{out}/v_{in} (intuitively)

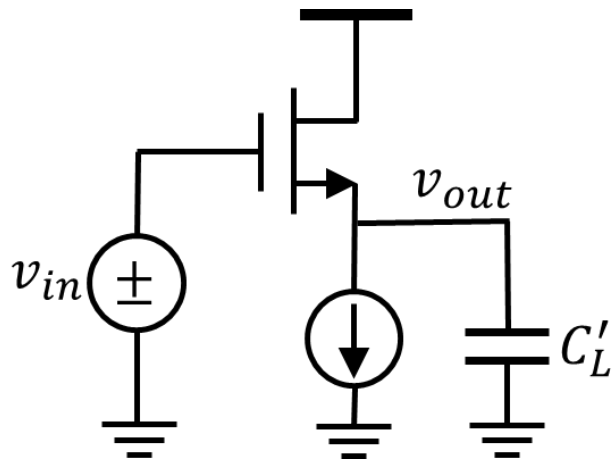

□ neglecting r_o and g_{mb} will give us ideal buffer $A_o = 1$

$$\square A_o = \frac{g_m r_o}{1 + (g_m + g_{mb}) r_o}$$

□ C_{gs} has a LHP feedforward zero $S_Z = -g_m / C_{gs}$


□ When calculating poles C_{gs} **isn't floating anymore!** (v_{in} is deactivated)

$$\square C_{out} = C'_L // C_{gs} \quad R_{out} = 1/g_m$$

(LHP feedforward zero)


$$\square \frac{v_{out}}{v_{in}} = \underbrace{\frac{g_m r_o}{1 + (g_m + g_{mb}) r_o}}_{A_o} \cdot \frac{\overbrace{1 + s \frac{C_{gs}}{g_m}}^{\text{(LHP feedforward zero)}}}{\underbrace{1 + \frac{s(C_{gs} + C'_L)}{g_m}}_{\text{output pole}}}$$

v_{out}/v_{in} (exact)

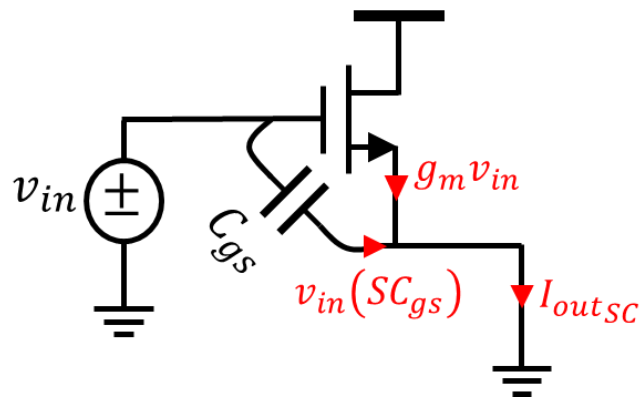

$$I_{out_{SC}} = g_m v_{in} + v_{in}(sC_{gs})$$

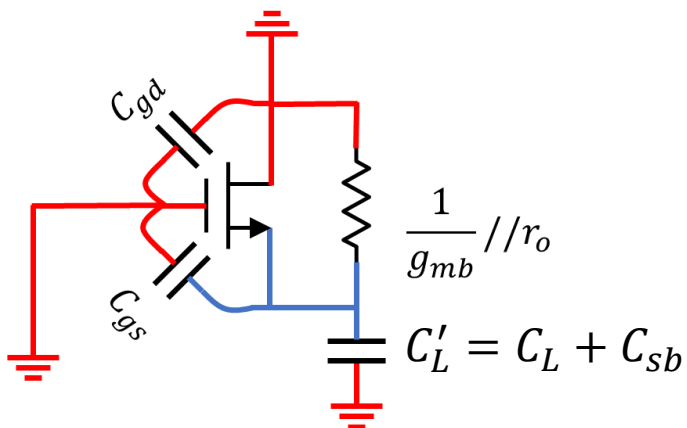
$$G_m = g_m \left(1 + s \frac{C_{gs}}{g_m} \right)$$



$$Z_{out} = \frac{1}{g_m} // r_o // \frac{1}{g_{mb}} // \frac{1}{s(C_{gs} + C'_L)} = \frac{1}{s(C_{gs} + C'_L) + g_m + g_{mb} + 1/r_o}$$

$$\frac{v_{out}}{v_{in}} = \frac{g_m r_o}{1 + (g_m + g_{mb})r_o} \times \frac{1 + s \frac{C_{gs}}{g_m}}{1 + \frac{s(C_{gs} + C'_L)}{g_m + g_{mb} + 1/r_o}}$$

Z_{in}

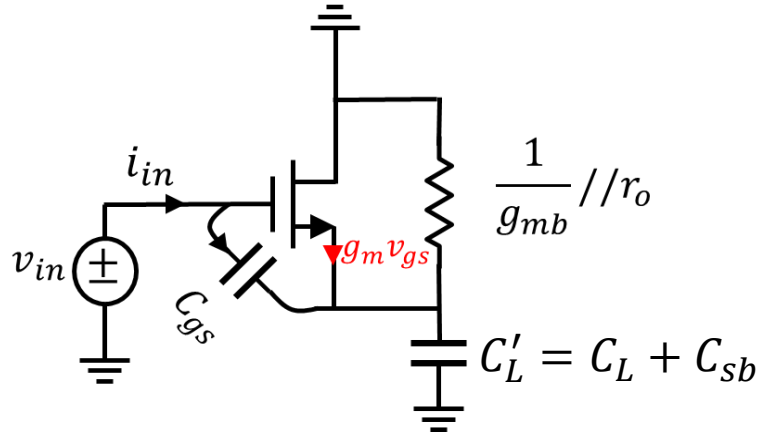

$$v_{in} = \frac{i_{in}}{sC_{gs}} + \left(i_{in} + i_{in} \frac{g_m}{sC_{gs}} \right) Z_s = \frac{i_{in}}{sC_{gs}} + \frac{i_{in} \left(1 + \frac{g_m}{sC_{gs}} \right)}{g_{mb} + 1/r_o + sC'_L}$$

$$Z_{in} = \frac{s(C_{gs} + C'_L) + g_m + g_{mb} + 1/r_o}{sC_{gs}(g_{mb} + 1/r_o + sC'_L)}$$

- ❑ Neglecting CLM and body effect $Z_{in} \approx \frac{1 + \frac{s(C_{gs} + C'_L)}{g_m}}{\frac{s^2 C_{gs} C'_L}{g_m}}$
- ❑ s^2 indicates negative impedance
- ❑ C_{gd} Shunts Z_{in} at high frequency



$$\frac{v_{out}}{v_{sig}}$$

$$\frac{v_{out}}{v_{sig}} = \frac{v_{out}}{v_{in}} \times \frac{Z_{in}}{Z_{in} + R_{sig}} = A_o \frac{1 + s \frac{C_{gs}}{g_m}}{1 + \frac{S(C_{gs} + C'_L)}{g_m}} \times \frac{1 + \frac{S(C_{gs} + C'_L)}{g_m}}{\frac{S^2 C_{gs} C'_L}{g_m} R_{sig} + \frac{S(C_{gs} + C'_L)}{g_m} + 1}$$

$$A(s) = A_o \frac{1 + s \frac{C_{gs}}{g_m}}{\frac{S^2 C_{gs} C'_L}{g_m} R_{sig} + \frac{S(C_{gs} + C'_L)}{g_m} + 1} \equiv \frac{A_o \left(1 + \frac{s}{\omega_z}\right)}{\frac{S^2}{\omega_n^2} + \frac{S}{\omega_n Q} + 1}$$

$$\omega_n = \sqrt{\frac{g_m}{R_{sig} C_{gs} C'_L}} \quad Q = \frac{\sqrt{g_m R_{sig} C_{gs} C'_L}}{C_{gs} + C'_L} \approx \sqrt{\frac{g_m R_{sig} C_{gs}}{C'_L}}$$


compensation network

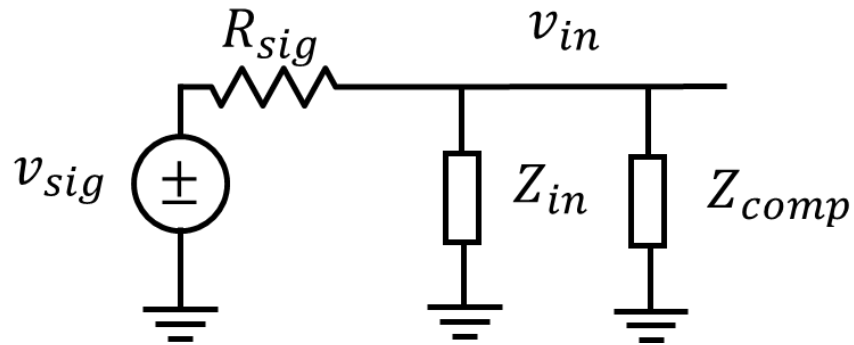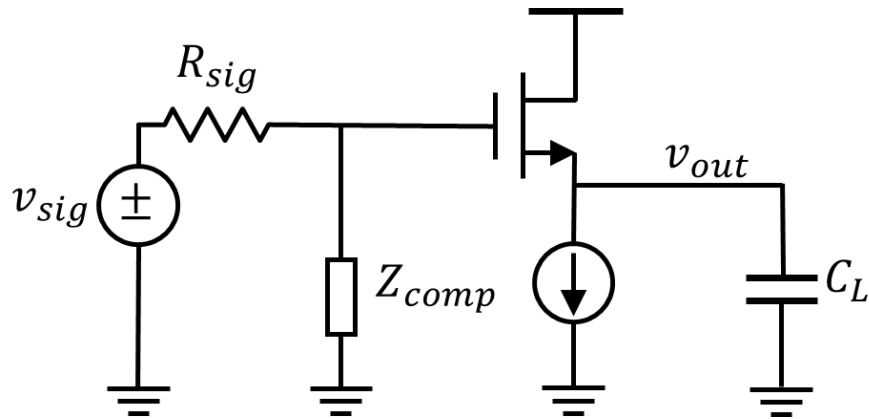

❑ We can eliminate the negative impedance by adding a compensation network

❑ $Z_{in_{new}} = Z_{in} // Z_{comp}$

❑ $Y_{in_{new}} = Y_{in} + Y_{comp}$

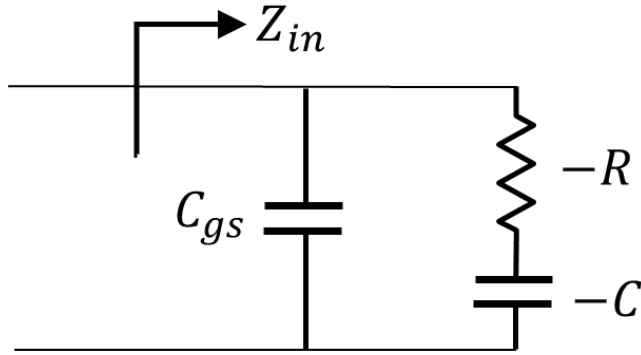

$$Z_{in} \approx \frac{SC'_L + g_m + g_{mb} + 1/r_o}{S^2 C_{gs} C'_L + SC_{gs}(g_{mb} + 1/r_o)} \quad C_L \gg C_{gs}$$

$$Y_{in} \approx \frac{S^2 C_{gs} C'_L + SC_{gs}(g_{mb} + 1/r_o)}{SC'_L + g_m + g_{mb} + 1/r_o} = SC_{gs} - \frac{SC_{gs}g_m}{SC'_L + g_m + g_{mb} + 1/r_o}$$

$$Y_{in} = SC_{gs} - \frac{1}{\frac{C'_L}{g_m C_{gs}} + \frac{g_m + g_{mb} + 1/r_o}{SC_{gs}g_m}} \equiv SC_{gs} - \frac{1}{R + \frac{1}{SC}}$$

□ equivalent to a capacitor // negative impedance

$$R = \frac{C'_L}{C_{gs}} \times \frac{1}{g_m}$$

$$C = \frac{g_m r_o}{1 + (g_m + g_{mb})r_o} C_{gs} = A_0 C_{gs}$$

